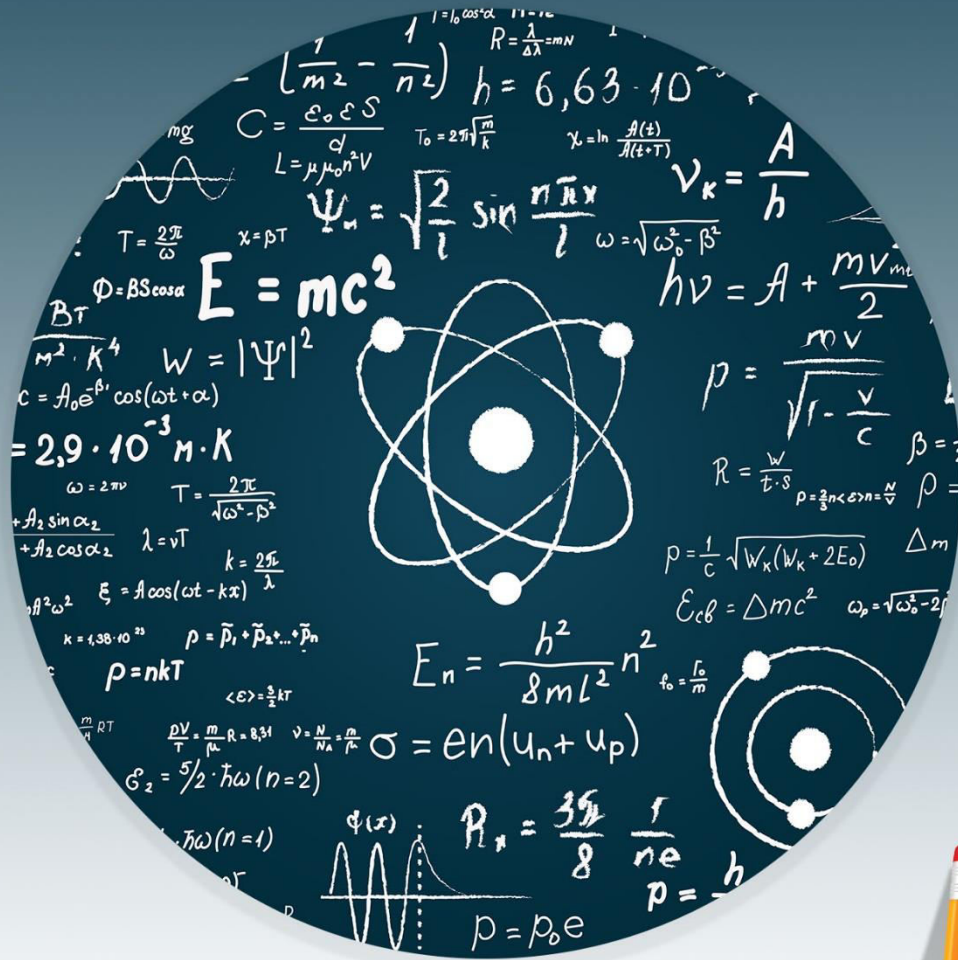


# PHYSICS



## WORKSHEET-2



**ST  P**

A PROJECT BY PUNJAB GROUP





## Worksheet-02

**Topics:-** Capacitor, Capacitance of a capacitor and its unit, Energy stored in a capacitor, Charging and discharging a capacitor, Polarization of dielectric of a capacitor

Q.1 A capacitor is a:

- A) Two terminal passive device
- B) Electric energy storing device
- C) Electric charge storing device
- D) All of these

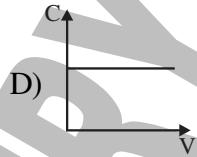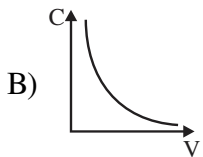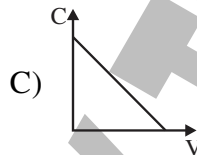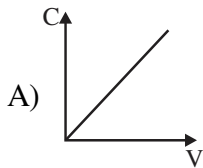Q.2 In the relation  $C = \frac{Q}{V}$ , the graph between "C" and "V" when no dielectric is placed is:



Q.3 The capacitance of capacitor does not depend on:

- A) Area of plates
- B) Distance between plates
- C) Geometry of plates
- D) Thickness of plates

Q.4 If area of plates of capacitor is doubled & distance between them is also doubled then capacitance:

- A) Is doubled
- B) Is halved
- C) Remains unchanged
- D) Is increased by four times

Q.5 A capacitor has a capacitance of  $10\mu\text{F}$  when there is a dielectric of dielectric constant 2 between its plates. If the dielectric is removed then capacitance becomes:

- A)  $20\mu\text{F}$
- B)  $5\mu\text{F}$
- C)  $10\mu\text{F}$
- D)  $40\mu\text{F}$

Q.6 The potential difference between capacitor plates is 10 V when there is a dielectric slab with  $\epsilon_r = 2$  between its plates. If slab is removed now potential difference is:

USE THIS SPACE FOR  
SCRATCH WORK

- A) 20 V
- B) 5 V
- C) 10 V
- D) 40 V

**Q.7** If the numerical value of area of each plate is equal to distance between parallel plates of a condenser (capacitor), then capacitance is equal to:

USE THIS SPACE FOR SCRATCH WORK

- A)  $\frac{2}{\epsilon_0}$
- B)  $2\epsilon_0$
- C)  $\epsilon_0$
- D)  $\frac{1}{\epsilon_0}$


**Q.8** Which one is true expression to find the series equivalent capacitance?

- A)  $\frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$
- B)  $C_e = \frac{C}{n}$  (n = No. of capacitors of equal capacitances, C = Capacitance of one capacitor)
- C)  $C_e = \frac{C_1 C_2}{C_1 + C_2}$
- D) All of these

**Q.9** When two capacitors of equal capacitances are connected in series their effective capacitance is  $C_s$ . Now if they are connected in parallel their effective capacitance becomes  $C_p$ , then  $C_s:C_p$  is:

- A) 2:1
- B) 1:2
- C) 4:1
- D) 1:4

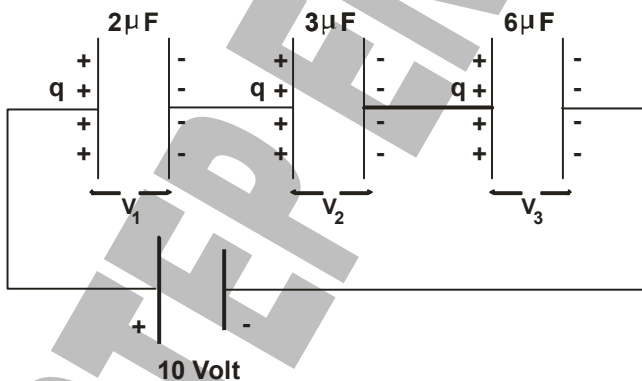**Q.10** The equivalent capacitance in the circuit shown is:



- A)  $1\mu F$
- B)  $2\mu F$
- C)  $\frac{1}{2}\mu F$
- D)  $3\mu F$


**Q.11** Referring to circuit shown in previous question, what is the charge stored on capacitor with capacitance  $3\mu F$  :



- C) Two in series and one in parallel
- D) Two in parallel and one in series


**Q.18** The effective capacitance between A & B in given circuit is:

USE THIS SPACE FOR SCRATCH WORK

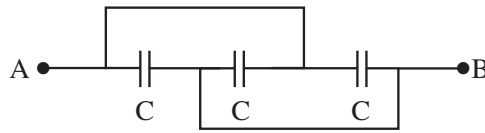

- A) C
- B) 2C
- C) 3C
- D)  $\frac{C}{2}$

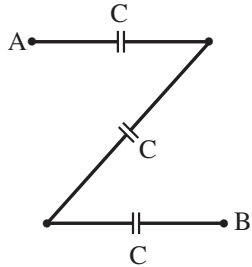**Q.19** The effective capacitance between A & B in given circuit is:



- A) 3C
- B)  $\frac{C}{3}$
- C)  $\frac{2C}{3}$
- D)  $\frac{3C}{2}$

**Q.20** Which one is not the expression of energy stored in a capacitor?

- A)  $\frac{1}{2}CV^2$
- B)  $\frac{1}{2}QV$
- C)  $\frac{1}{2} \frac{Q^2}{C}$
- D)  $\frac{1}{2}E^2 \epsilon_0 \epsilon_r$

**Q.21** A capacitor stores \_\_\_\_\_ energy in it \_\_\_\_\_ field.

- A) Gravitational Potential, Gravitational
- B) Electric Potential, Electric
- C) Magnetic Potential, Magnetic
- D) None of these

**Q.22** If the electric field strength is doubled, the energy stored in capacitor becomes:

- A) Double
- B) Half
- C) Remains same
- D) Four times

**Q.23** If a dielectric slab of dielectric constant  $\epsilon_r$  is placed between plates of a charged capacitor, the energy stored:

- A) Decreases
- B) Increases
- C) Remains same
- D) None of these

**Q.24** In the charging circuit of a capacitor if the value of capacitance is increased, then capacitor charges:

- A) Slowly
- B) Rapidly
- C) At same speed
- D) None of these


**Q.25 Capacitor charges or discharges:**

- A) Linearly with time
- B) Exponentially with time
- C) Sinusoidally with time
- D) None of these

**Q.26 “ $\frac{t}{RC}$ ” has the dimensions same as that of:**

- A) Time
- B) Strain
- C) Frequency
- D) Capacitance

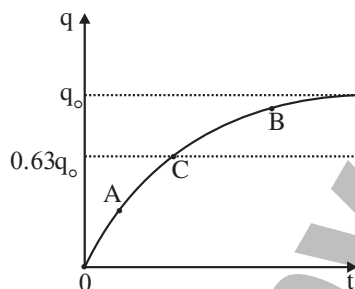**Q.27 In the following charging curve of capacitor what does the slope represent?**



- A) Capacitance
- B) Charge stored
- C) Current passing
- D) Voltage


**Q.28 Referring to the Question # 27, the value of current will be maximum at:**

- A) Point A
- B) Point B
- C) Point C
- D) Same at all points

**Q.29 Referring to Question # 27, the charging speed of capacitor is maximum at:**

- A) Point A
- B) Point B
- C) Point C
- D) Same at all points

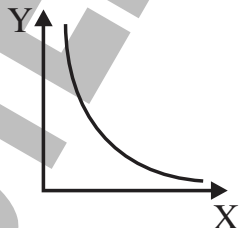**Q.30 What physical quantities may X and Y represent? (Y represents the first mentioned quantity):**



- A) Electric Intensity vs charge
- B) Kinetic energy vs velocity of particle

USE THIS SPACE FOR SCRATCH WORK

- C) Capacitance vs charge to give a constant potential
- D) Potential vs capacitance to give a constant charge

STEP ENTRY TEST 2021

**ANSWER KEY (Worksheet-02)**

1	D	11	C	21	B
2	D	12	D	22	D
3	D	13	C	23	A
4	C	14	B	24	A
5	B	15	D	25	B
6	A	16	B	26	B
7	C	17	C	27	C
8	D	18	C	28	A
9	D	19	B	29	A
10	A	20	D	30	D

**SOLUTIONS****Unit – 6 (WS-02)**

**Q.1** Answer is “D”

**Solution:-** “A capacitor is a two terminal passive device which stores electric potential energy (due to charge storage) in its electric field”.

**Q.2** Answer is “D”

**Solution:-** In the absence of dielectric “C” remains same whenever “V” changes.

**Q.3** Answer is “D”

**Solution:-** Capacitance does not depend on:

- (i) Thickness of plates
- (ii) Metal of plates

**Q.4** Answer is “C”

**Solution:-**  $C = \frac{A\epsilon_0}{d}$

**Q.5** Answer is “B”

**Solution:-**  $C_{med} = \epsilon_r C_{vac}$

**Q.6** Answer is “A”

**Solution:-**  $V_{med} = \frac{V_{vac}}{\epsilon_r}$

**Q.7** Answer is “C”

**Solution:-**  $C_{vac} = \frac{A\epsilon_0}{d}$

**Q.8** Answer is “D”

**Solution:-** We must remember that the formula's for combination of capacitors are inverse of that for the resistances, so in series combination if we have number of unequal capacitors then we use;

$$\bullet \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

• For just two unequal capacitors we use;

$$C_{eq} = \frac{\text{Product of capacitances}}{\text{Sum of capacitances}} = \frac{C_1 C_2}{C_1 + C_2}$$

**Q.9** Answer is “D”

**Solution:-**  $C_P = nC$ ;  $C_S = C/n$

**Q.10** Answer is “A”

**Solution:-**  $\frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$

**Q.11** Answer is “C”

**Solution:-**  $Q = C_e V$

**Q.12** Answer is “D”

**Solution:-** Because of electric polarization of dielectric;

- Charge stored on plates remains same.
- Effective area of plates increases.
- Surface charge density decreases  $\left( \sigma = \frac{Q}{A_{eff}} \right)$
- Electric field strength decreases  $\left( E = \frac{\sigma}{\epsilon} \right)$
- Potential difference between plates decreases ( $V = Ed$ )



- Capacitance increases  
 $(C_{med} = \epsilon_r C_{vac})$

**Q.13 Answer is “C”**

**Solution:-** Because of electric polarization of dielectric;

- Charge stored on plates remains same.
- Effective area of plates increases.
- Surface charge density decreases  
 $(\sigma = \frac{Q}{A_{eff}})$
- Electric field strength decreases  
 $(E = \frac{\sigma}{\epsilon})$
- Potential difference between plates decreases ( $V = Ed$ )
- Capacitance increases  
 $(C_{med} = \epsilon_r C_{vac})$

**Q.14 Answer is “B”**

**Solution:-** Start simplifying circuit form top right corner

**Q.15 Answer is “D”**

**Solution:-**  $V_{net} = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$

**Q.16 Answer is “B”**

**Solution:-** For series capacitors

$$V_1 = \left( \frac{C_2}{C_1 + C_2} \right) V, V_2 = \left( \frac{C_1}{C_1 + C_2} \right) V$$

**Q.17 Answer is “C”**

**Solution:-**  $C_e = (2) + \left( \frac{2 \times 2}{2+2} \right)$

**Q.18 Answer is “C”**

**Solution:-** All capacitors are in parallel

**Q.19 Answer is “B”**

**Solution:-** All capacitors are in series

**Q.20 Answer is “D”**

**Solution:-** “ $\frac{1}{2} E^2 \epsilon_r \epsilon_0$ ” is the relation for energy density means energy per unit volume but not just energy.

**Q.21 Answer is “B”**

**Solution:-** Capacitor stores electric potential energy in the form of electric field (E) between the two plates of capacitor, can be seen in following relation;

$$Energy = \frac{1}{2} Ad \epsilon_r \epsilon_0 E^2$$

**Q.22 Answer is “D”**

**Solution:-** Energy  $\propto E^2$

**Q.23 Answer is “A”**

**Solution:-** By placing medium  $C \uparrow, V \downarrow$  as

Energy =  $\frac{1}{2} CV^2$  Since power of V is greater than C, so “V” decides energy trend.

**Q.24 Answer is “A”**

**Solution:-**  $\uparrow t = RC \uparrow$

Greater the value of time constant, slower will be the charging speed.

**Q.25 Answer is “B”**

**Solution:-** Discharging equation  $\Rightarrow$

$$q = q_0 e^{-\frac{t}{RC}}$$

**Q.26 Answer is “B”**

**Solution:-** RC has units of time

**Q.27 Answer is “C”**

**Solution:-** Slope =  $\frac{\Delta y}{\Delta x} = \frac{\Delta q}{\Delta t} = I$

**Q.28 Answer is “A”**

**Solution:-**  $I = \text{Slope} \rightarrow \text{Maximum}$  at starting point A

**Q.29** Answer is “A”

**Solution:-**  $I \propto \text{Slope} \propto \text{Charging speed}$

**Q.30** Answer is “D”

**Solution:-** When  $Q = \text{Constant}$  and we try dielectrics of different  $\epsilon_r$  between capacitor plates, then;  $V \propto \frac{1}{C}$

STEP ENTRY TEST 2021

# STOP

A PROGRAM BY PUNJAB GROUP

