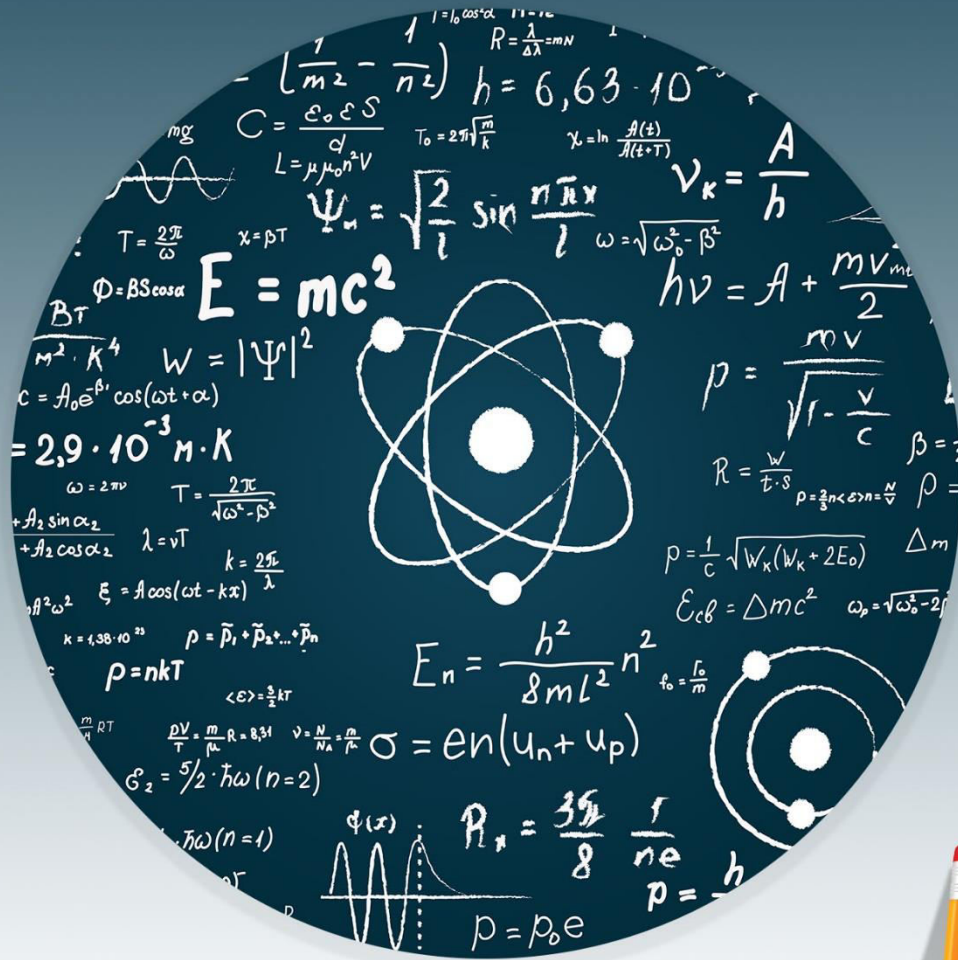


PHYSICS



WORKSHEET-3



ST  P


A PROJECT BY PUNJAB GROUP

Worksheet-03

Topics:- Current, Ohm's Law, Specific resistance, Effect of temperature on resistance, Temperature coefficient of resistance

- Q.1** The graphical representation of ohm's law is:
 A) Hyperbola C) Parabola
 B) Ellipse D) Straight Line
- Q.2** ohm is defined as:
 A) volt / ampere C) ampere / volt
 B) volt / coulomb D) joule / coulomb
- Q.3** The resistance of a meter cube of the substance is called:
 A) Resistivity C) Permittivity
 B) Conductivity D) None of these
- Q.4** The S.I unit of resistivity is:
 A) ohm-m C) ohm-m³
 B) ohm-m² D) ohm-cm
- Q.5** When the resistances are connected in series the equivalent resistance is equal to?
 A) Sum of the reciprocal of the individual resistances
 B) Sum of individual resistances
 C) Product of the individual resistances
 D) Can't be predicted
- Q.6** The potential difference across resistances in series combination is:
 A) Always same C) May be same or different
 B) Always different D) None of these
- Q.7** Three resistances 500 ohm, 350 ohm and 500 ohm are connected in series the equivalent resistance will be:
 A) 1300 Ω C) 650 Ω
 B) 1350 Ω D) 1400 Ω

Q.8 In the circuit shown

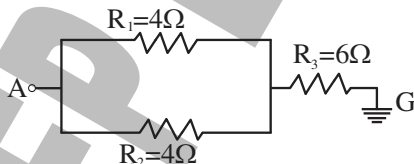

If voltage applied at A is 20 V then what would be the resultant current passing through R₃.

- A) 4 A C) 2.5 A
 B) 6 A D) 10 A
- Q.9** If a battery of 9 V is connected across 2.0 Ω resistance, then what would be the resultant current?
 A) 4.0 A C) 3.5 A
 B) 4.5 A D) 5.0 A


USE THIS SPACE FOR
SCRATCH WORK

Q.10 How many different resistances are possible with two equal resistors?

- A) 2
B) 3
C) 4
D) 5

**USE THIS SPACE FOR
SCRATCH WORK**

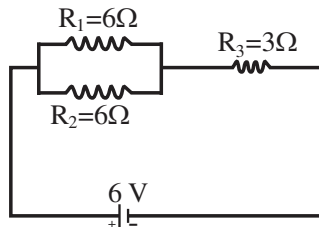Q.11 Find the equivalent resistance of the circuit:



- A) 3 Ω
B) 12 Ω
C) 6 Ω
D) 4 Ω

Q.12 Referring to Q.11, the total current drawn from source is:

- A) 0.5 A
B) 2 A
C) 1 A
D) 0.25 A

Q.13 Referring to Q.11, the current passing through R1 is:

- A) 0.5 A
B) 2 A
C) 1 A
D) 0.25 A

Q.14 Referring to Q.11, the current passing through R2 is:

- A) 0.5 A
B) 2 A
C) 1 A
D) 0.25 A

Q.15 Referring to Q.11, the current passing through R3 is:

- A) 0.5 A
B) 2 A
C) 1 A
D) 0.25 A


Q.16 2×10^6 electrons pass through a conductor in 1 ms. Find electric current flowing through conductor:

- A) 32×10^{-9} A
B) 32×10^{-10} A
C) 3.2×10^{-10} A
D) 0.32×10^{-10} A

Q.17 A carbon resistor is connected to a battery of 50 V and 2 A current is passing through it. If voltage is increases to 75 V, the current will become:

- A) 3 A
B) 1.5 A
C) 4.5 A
D) 6 A

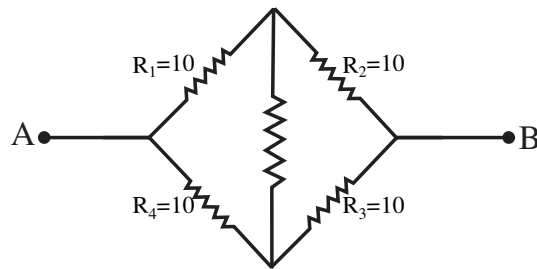Q.18 If the resistance of each resistor is 10 ohm in the following figure, then what will be the effective resistance between points 'A' and 'B':



USE THIS SPACE FOR
SCRATCH WORK

- A) 40 ohm
B) 50 ohm
- C) 30 ohm
D) 10 ohm

Q.19 The ratio of effective resistances of two identical resistors, first connected in series then in parallel is:

- A) 1:2
B) 2:1
- C) 4:1
D) 1:4

Q.20 A wire carrying electronic current is:

- A) Negatively charged
B) Positively charged
- C) Electrically neutral
D) Any of these

STEP ENTRY TEST 2021

ANSWER KEY (Worksheet-03)			
1	D	11	C
2	A	12	C
3	A	13	A
4	A	14	A
5	B	15	C
6	C	16	C
7	B	17	A
8	C	18	D
9	B	19	C
10	B	20	C

SOLUTIONS

Unit – 7 (WS-03)

Q.1 Answer is “D”

Solution:- Graph of ohm’s law is between “V” and “I”. Since $V \propto I$, so, graph is straight line inclined with “V-axis”.

Q.2 Answer is “A”

Solution:- By ohm’s law:

$$R = \frac{V}{I}$$

$$1 \text{ ohm} = \frac{1 \text{ volt}}{1 \text{ ampere}}$$

Q.3 Answer is “A”

Solution:- Resistivity of material of wire is defined as:

$$\rho = \frac{RA}{L} \quad \rho = \frac{R(1 \text{ m}^2)}{(1 \text{ m})}$$

Q.4 Answer is “A”

Solution:- By formula

$$\rho = \frac{RA}{L} = \frac{\Omega \text{ m}^2}{\text{m}} = \Omega \text{ m}$$

Q.5 Answer is “B”

Solution:- $R_e = R_1 + R_2 + R_3 + \dots$

Q.6 Answer is “C”

Solution:- If resistances are same then potential is also same, otherwise it is different.

Q.7 Answer is “B”

Solution:- $R_e = R_1 + R_2 + R_3$

Q.8 Answer is “C”




Solution:- $I = \frac{V}{R_e}$

Q.9 Answer is “B”

Solution:- $I = \frac{V}{R}$

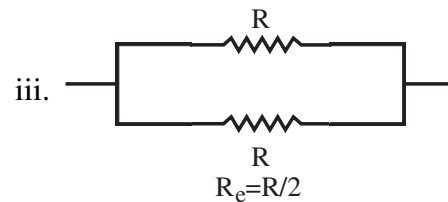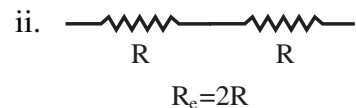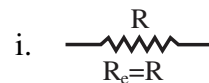Q.10 Answer is “B”

Solution:- By two resistors of equal value, following different resistances can be obtained:



Q.11 Answer is “C”

Solution:- $R_e = (R_1 \parallel R_2) + R_3$

Q.12 Answer is “C”

Solution:- $V = I R_e$

Q.13 Answer is “A”

Solution:- $I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I$

Q.14 Answer is “A”

$$\text{Solution:- } I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I$$

Q.15 Answer is “C”

$$\text{Solution:- } I_3 = I_1 + I_2$$

Q.16 Answer is “C”

Solution:-

Use:

$$I = \frac{Q}{t} = \frac{ne}{t}$$

Q.17 Answer is “A”

Solution:-

Initially

$$V = IR$$

$$R = \frac{V}{I} = \frac{50}{2} = 25 \Omega$$

After increasing voltage

$$I' = \frac{V'}{R} = \frac{75}{25} = 3 \text{ A}$$

Q.18 Answer is “D”

Solution:-

$$R_{AB} = (10 + 10) \parallel (10 + 10)$$

Q.19 Answer is “C”

Solution:-

$$R_s = nR$$

$$R_p = \frac{R}{n}$$

Taking ratio

$$\frac{R_s}{R_p} = \frac{nR}{\frac{R}{n}} = n^2$$

Q.20 Answer is “C”

Solution:-

Any current carrying object is electrically neutral.

STOP

A PROGRAM BY PUNJAB GROUP

